




# SPO2 Project


**Muhammad Athar &  
Jason Huang**
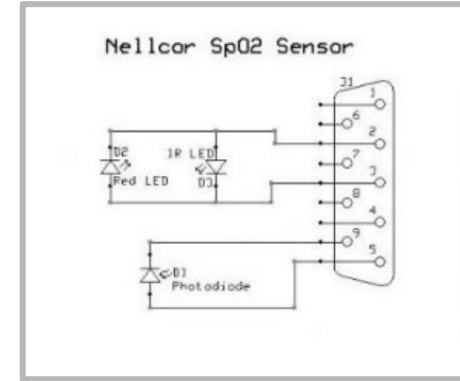
# Brief Overview

- ❑ Requirements and Constraints
- ❑ High Level Model
- ❑ Individual Subcircuits
- ❑ Arduino
- ❑ Validation



*SpO<sub>2</sub> Sensor Pinout*

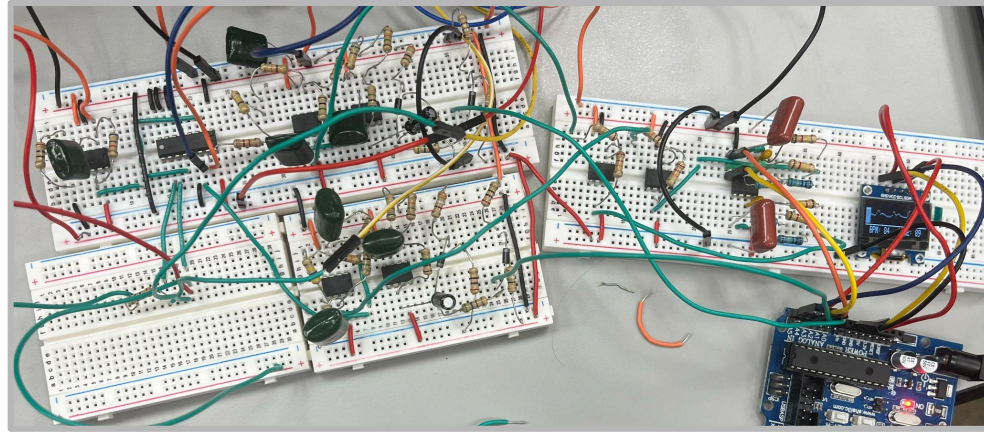

*Final Working Product*

# Design Requirements & Constraints


## Requirements

- ❑ Display the heartbeat waveform, BPM, and % SPO<sub>2</sub> of an individual on an OLED Display.

## Constraints


- ❑ Use of Nellcor Ds-100A SpO<sub>2</sub> sensor, DB9 breakout board, OLED display, and CD4053BE analog multiplexer IC.
- ❑ Limit LED current to  $< 15\text{mA}$ .
- ❑ Reverse-Biased Photodiode.

# High Level Model

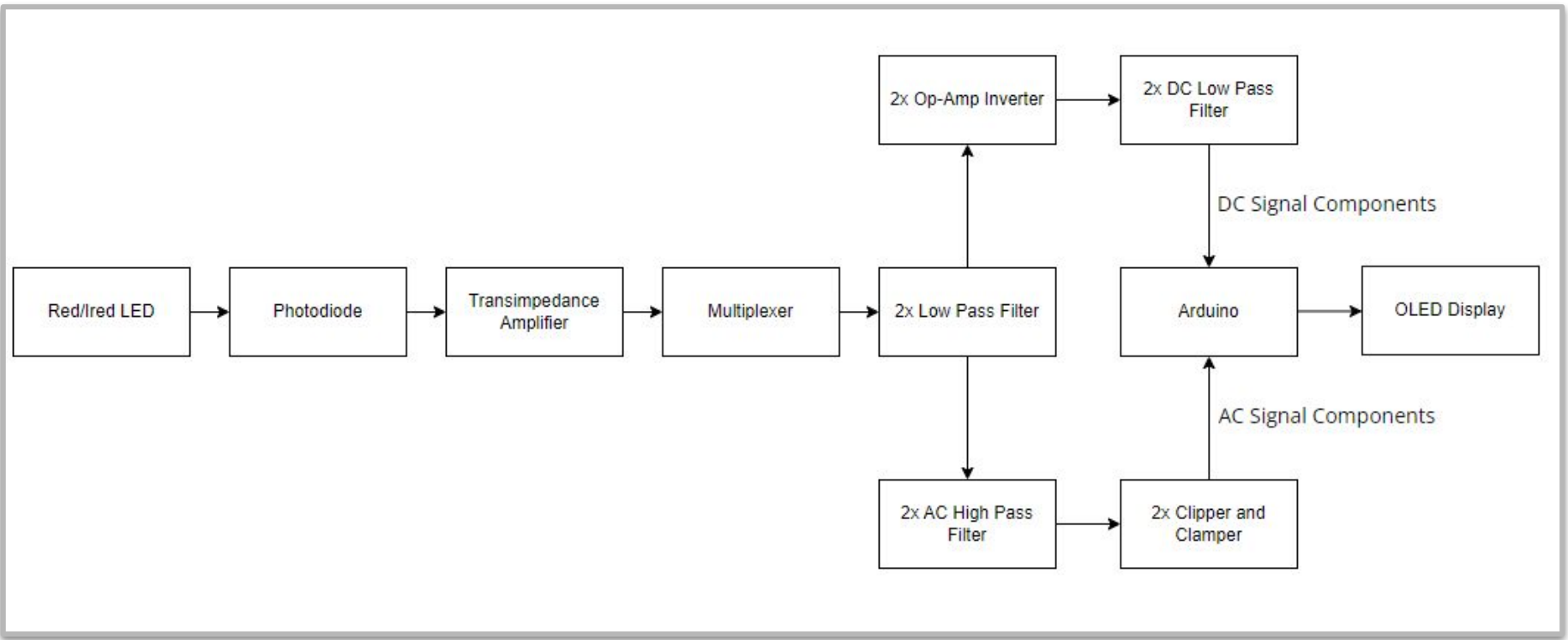

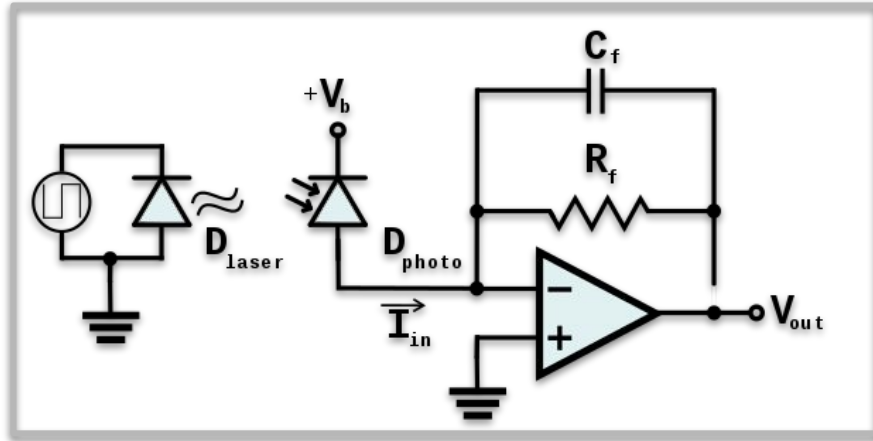
# Transimpedance Amplifier

- ❑ Converts photodiode-produced current from alternating LEDs (500hz) into voltage.
- ❑ Gain =  $R_f = 6.8k$
- ❑ Output is the input to **MUX**.




*TIA Schematic*

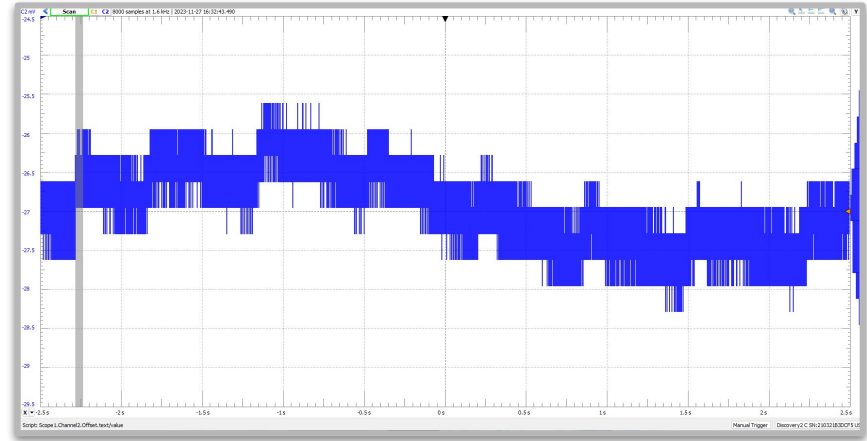


*TIA Output*
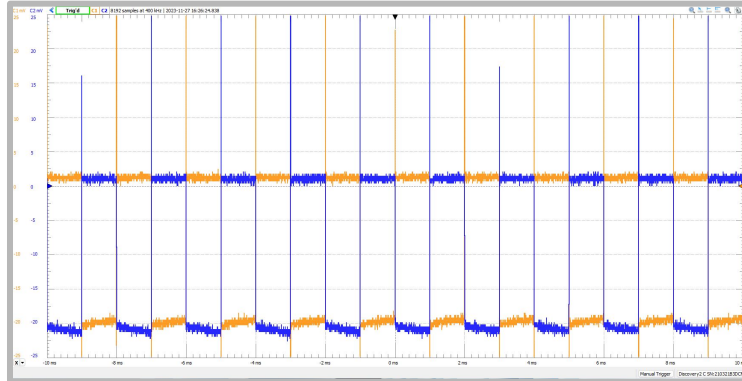
# Multiplexer

- ❑ 3x 2-1 Multiplexers
- ❑ Splits the circuit into Red & Infrared Sections.
- ❑ Alternate signals at 500 Hz



*MUX Output*

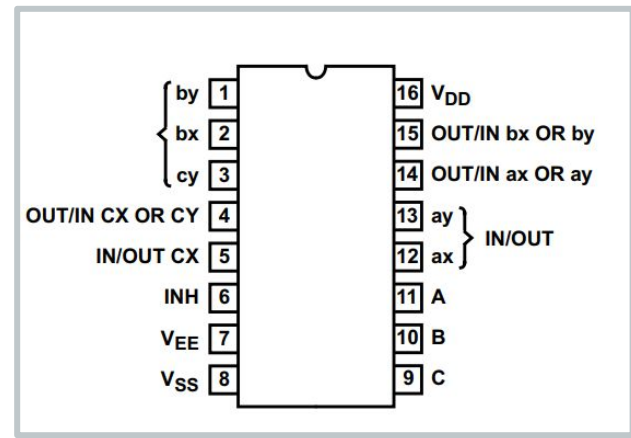


*MUX Schematic*


INPUT STATES				ON CHANNEL(S)
INHIBIT	C	B	A	
CD4051B				
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	X	X	X	None
CD4052B				
0		0	0	0x, 0y
0		0	1	1x, 1y
0		1	0	2x, 2y
0		1	1	3x, 3y
1		X	X	None
CD4053B				
0	X	X	0	ax
0	X	X	1	ay
0	X	0	X	bx
0	X	1	X	by
0	0	X	X	cx
0	1	X	X	cy
1	X	X	X	None

*MUX Truth Table*


# AC Filtration Circuit

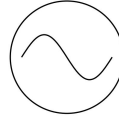

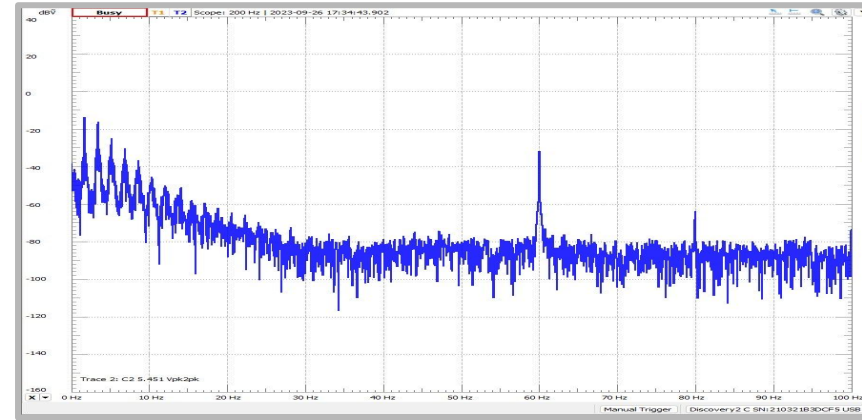- ❑ **LPF (Reduces Signal Noise)**
  - ❑ Break Frequency @ 5 Hz.
    - ❑  $0.67 \text{ Hz} < f < 2 \text{ Hz}$ .
  - ❑ Gain = 50.
  - ❑ Keeps Harmonics.
  - ❑ Attenuates 60hz human noise.
- ❑ **HPF (Centers Signal)**
  - ❑ Removes any DC offset.
    - ❑ Break Frequency @ 0.5 Hz.
  - ❑ Gain = 60.
  - ❑ Only passes heart-rate frequencies.
  - ❑ Output is the input to **Clipper & Clamper Circuit**.




*Spectrum before AC Filtration*

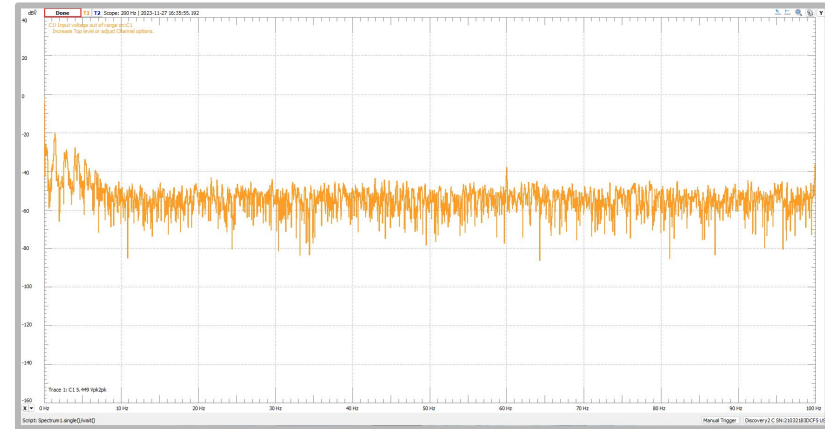


*Spectrum after AC Filtration*
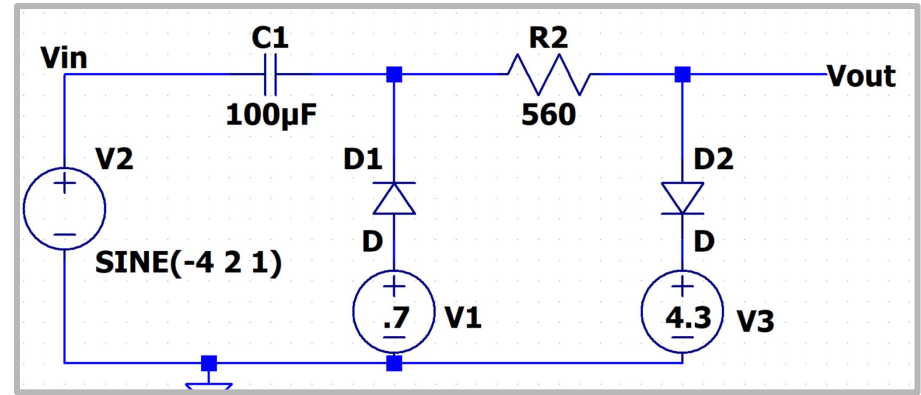
# Clipper & Clamper

- ❑ Clipper shifts signal above 0V
- ❑ Clamper clamps signal at +5V
- ❑ Safeguards the Arduino
- ❑ Output is the input to **Arduino**



*Clipper & Clamper Schematic*

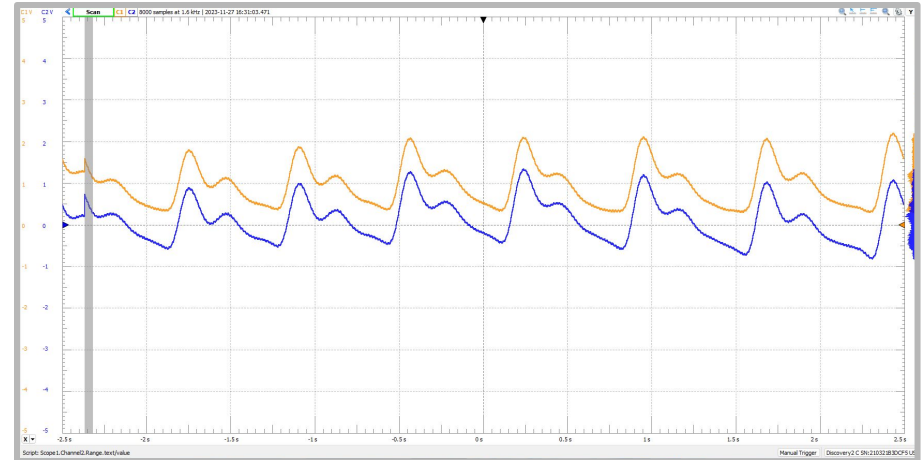


*Input vs Output*



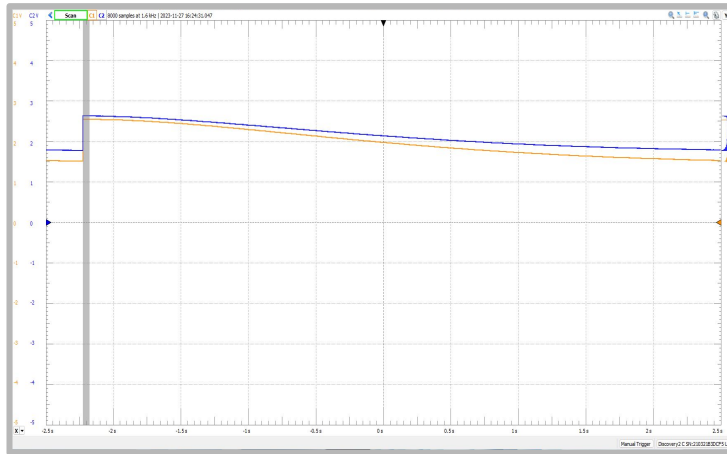
# DC Circuit


- ❑ Passes only 0Hz.
- ❑ Stems from AC LPF.
- ❑ Required to compute R.
- ❑ DCRed & DCIred are outputted.
- ❑ Output is an input to **Arduino**.



*Discharging DC*

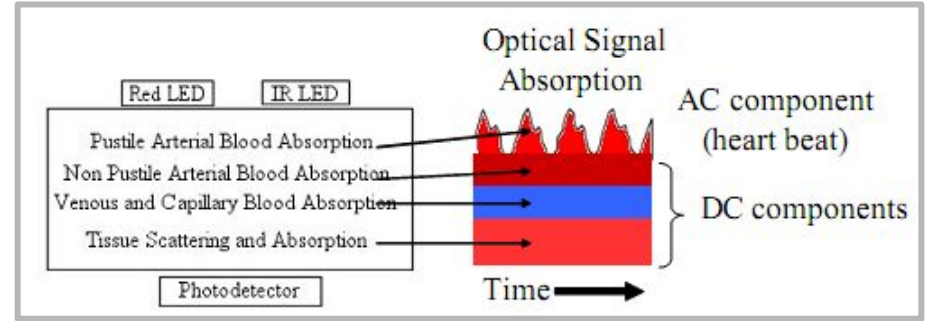

*AC vs DC Components*

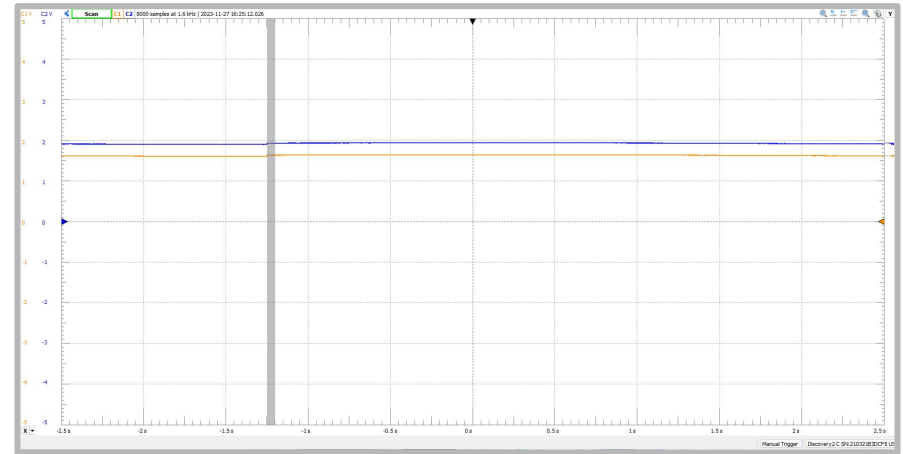


*DC Output*

# Arduino


- ❑ Reads the AC & DC output components.
- ❑ Computes R & % SpO<sub>2</sub>.
  - ❑ % SpO<sub>2</sub> = 110 - 25R
- ❑ Outputs to **OLED Display**
  - ❑ Heartbeat Signal
  - ❑ BPM (beats per minute)
  - ❑ % SPO<sub>2</sub>

$$R = \frac{\frac{AC_{red}}{DC_{red}}}{\frac{AC_{ired}}{DC_{ired}}}$$

*R equation*

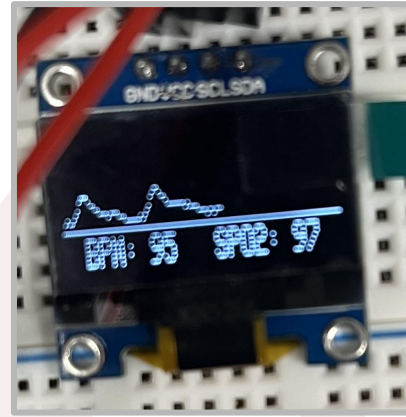

*OLED Display*

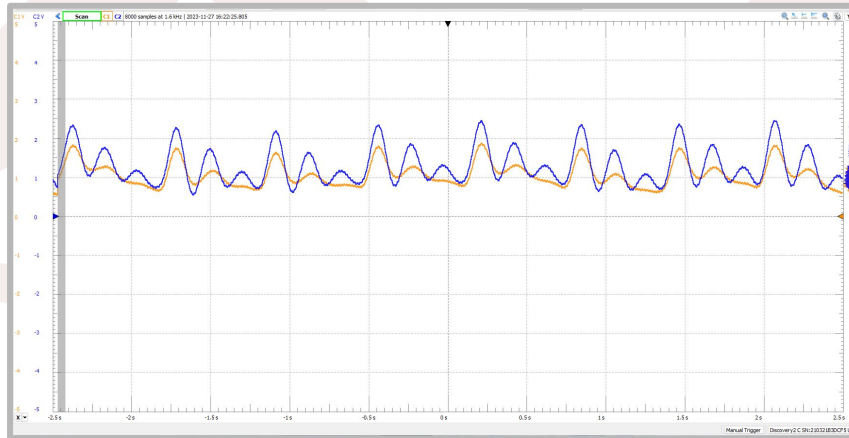

*AC Inputs to Arduino*

# Validation Tests

- ❑ Comparisons between Nellcor Ds-100A and Commercial SpO<sub>2</sub>.
- ❑ BPM and waveform are consistent.
- ❑ SpO<sub>2</sub> value is close, with minimal margins of error.
  - ❑ 80-100%
- ❑ Overall, it fulfilled the requirements under the given constraints!



*Nellcor vs Commercial Sensor*

Thanks For Listening!